



FYSIKUM

# Digital System Construction - 1

Lecture 3:  
More VHDL, intro to sequential logic

Instantiation/generics/generate

Operators in VHDL


Sequential logic

Introduction to Lab 2

# Component libraries

- FPGA design software organizes your VHDL modules (and other design units) in libraries
  - ◆ User-written design units are usually placed in a default library
    - ✦ In many design environments: “work”
    - ✦ In Xilinx Vivado: “xil\_defaultlib”
  - ◆ In larger or complex projects, multiple libraries from different sources can be imported to your project
    - ✦ Good for combining custom/shared code

# Libraries in Vivado

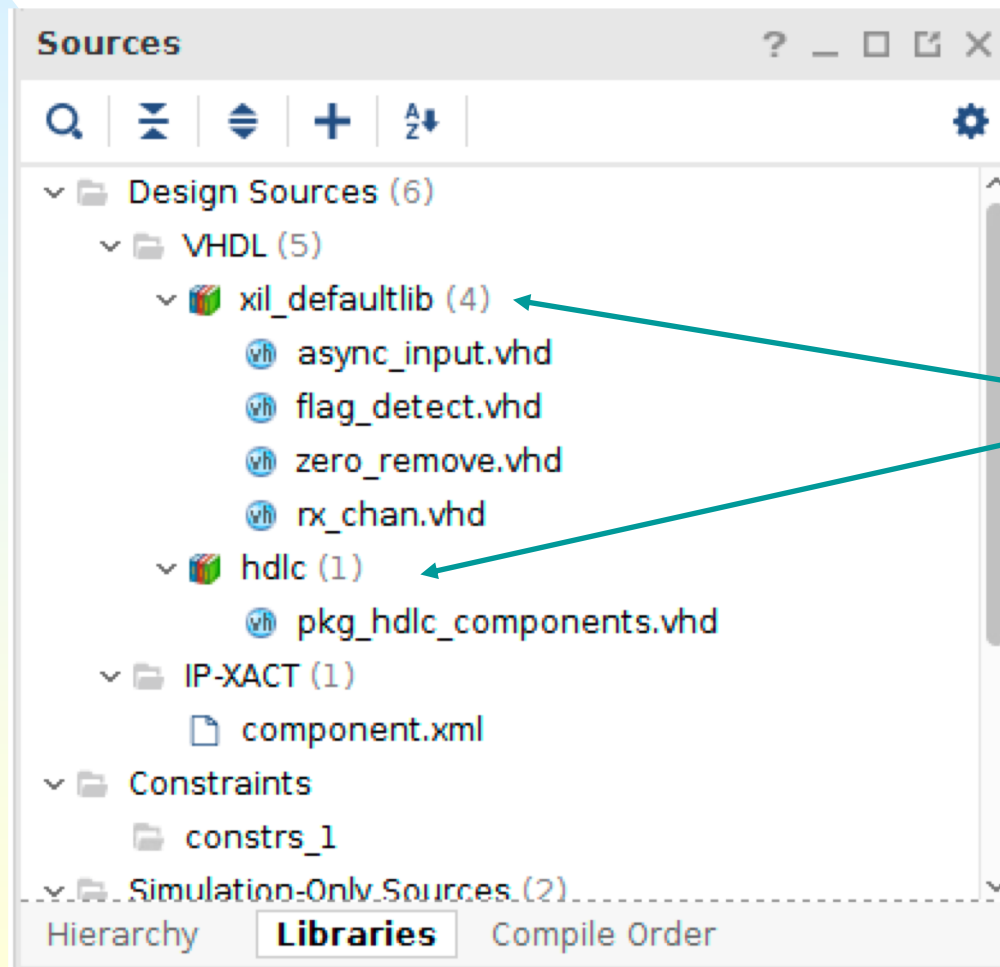

Two VHDL  
libraries

# Instantiating components

- The synthesis tool needs to know where to find a component.
- There are several options:
  - ◆ Declare a component, use a configuration statement to specify which library to use for it
    - ✦ (optionally entity/architecture as well)
  - ◆ Declare component without a configuration
    - ✦ Synthesis tool assumes the default library
  - ◆ Don't declare component, instantiate directly from library
    - ✦ This is called "Entity instantiation"

# With configuration

architecture arch of MuxExample is

```
component Mux
```

```
  port(  a:      in std_logic;  
        b:      in std_logic;  
        sel:    in std_logic;  
        y:      out std_logic  
  );
```

```
end component;
```

```
for all : Mux use entity work.Mux; -- Configuration
```


```
begin
```

```
  mux0: Mux
```

```
    port map (a=>a(0), b=>b(0), sel=>sel, y=>y(0));
```

```
end arch;
```

Library Entity

 

# More complete configuration

architecture arch of MuxExample is

```
component Mux
```

```
  port( a:    in std_logic;  
        b:    in std_logic;  
        sel:  in std_logic;  
        y:    out std_logic  
  );
```

```
end component;
```

```
for all : Mux use entity work.Mux(arch1); -- Configuration
```


```
begin
```

```
  mux0: Mux
```

```
    port map (a=>a(0), b=>b(0), sel=>sel, y=>y(0));
```

```
end arch;
```

Library Entity Architecture

 

# “Entity instantiation”

architecture arch of MuxExample is

**-- No component instantiation**

begin

    mux0 : **entity work.Mux -- use MUX from library work**

        port map (a=>a(0), b=>b(0), sel=>sel, y=>y(0));

end arch;

# Without configuration

architecture arch of MuxExample is

**component Mux**

```
    port(  a:      in std_logic;  
          b:      in std_logic;  
          sel:    in std_logic;  
          y:      out std_logic
```

```
    );
```

```
end component;
```

```
begin
```

```
    mux0: Mux  -- Use default library (e.g. work)
```

```
        port map (a=>a(0), b=>b(0), sel=>sel, y=>y(0));
```

```
end arch;
```



# Generics

- Generics are static values or parameters
  - ◆ Only used to guide synthesis
    - ✦ Nothing that changes in run time
  - ◆ Can be any valid type
    - ✦ Integer, Boolean, time, floating point, text...
    - ✦ User defined types may also be used
- How to declare and use generics
  - ◆ Declare in the entity
    - ✦ One or more, in a list format similar to ports
  - ◆ Must be declared with a default value
    - ✦ Can override that value during instantiation
  - ◆ Can be used in both the entity port declaration and the architecture

# Using generics

- Real-world examples:
  - ◆ Design units with customizable size/width
    - ✦ n-bit Adder/multiplexer/comparator/etc.
  - ◆ Register timing options
    - ✦ Choose rising/falling clock edge
  - ◆ Define initial register values, memory contents
    - ✦ Look-up tables
    - ✦ Random number generator “seed”
  - ◆ Set options for e.g. generate statements
    - ✦ (“if [generic] then....”)
- Very useful for writing portable/reusable code!

# Generic declaration

- Example from ATLAS trigger upgrade:

```
component ClusterSort is
  generic (output_width      : integer:= 5; --width of the sort output
          input_chan_width  : integer:= 20; --number of input channels
          input_tobs        : integer:= 120 ); --number of TOBs
  port   (clk40              : in std_logic; -- 40 MHz clock
          Iso_Mask           : in std_logic_vector (4 downto 0);
          InputArr           : in ClusterArray (input_tobs-1 downto 0);
          OutputArr          : out TOBArray (output_width-1 downto 0) );
end component;
```

Sorting algorithm with adjustable sizing

# Generate statement

- Generate is a concurrent loop statement
  - ◆ Used to replicate concurrent statements
- Has two forms
  - ◆ for: generates a fixed number of concurrent statements (most commonly used form)
    - ✦ **for i in 0 to 15 generate**
  - ◆ if: conditionally selects concurrent statements to be generated
    - ✦ **if i = 2 generate**
- Generate loops can be nested

# Example: n-bit MUX

- Use a **generic** integer in entity declaration to define the width of the inputs/outputs
- Use **generate** in the architecture to instantiate the right number of one-bit MUXes

# nx2 multiplexer entity

Generic `nmux_width` sets the port widths

```
entity MuxN2 is
generic (nmux_width : integer := 4;
        );
port(a:  in std_logic_vector (nmux_width-1 downto 0);
     b:  in std_logic_vector (nmux_width-1 downto 0);
     sel: in std_logic;
     y:  out std_logic_vector (nmux_width-1 downto 0)
);
end MuxN2;
```

*variable width*

# Nx2 mux architecture

## Generic nmux\_width used with generate

```
architecture arch of MuxN2 is
  component Mux
    port( a:      in std_logic;
          b:      in std_logic;
          sel:    in std_logic;
          y:      out std_logic
        );
  end component;

begin
  g0 : for i in 0 to (nmux_width-1) generate
    u1: Mux
      port map (a=>a(i), b=>b(i), sel=>sel, y=>y(i));
    end generate g0;
end arch;
```

1-bit MUX

# 4-bit adder (complicated)

```
architecture arch1 of add4 is
  component full_adder
    port( a, b, cin : in std_logic;
          cout, s: out std_logic);
  end component;
  signal carry_bit: std_logic_vector(3 downto 1);
begin
  four_adder : for i in 0 to 3 generate
    bottom_adder: if i = 0 generate
      a_bot : full_adder
      port map (a=>a(0), b=>b(0), cin=>carry_in,
               cout=>carry_bit(1), s=>s(0));
    end generate bottom_adder;
    middle_adders: if (i>0 and i<3) generate
      a_mid : full_adder
      port map (a=>a(i), b=>b(i), cin=>carry_bit(i),
               cout=>carry_bit(i+1), s=>s(i));
    end generate middle_adders,
    top_adder: if i = 3 generate
      a_top : full_adder
      port map (a=>a(3), b=>b(3), cin=>carry_bit(3),
               cout=>carry_out, s=>s(3));
    end generate top_adder;
  end generate four_adder;
end arch1;
```

FOR loop

Conditional

Conditional

Conditional



# 4-bit adder (simpler)

architecture arch1 of add4 is

```
component full_adder
    port(
        a, b, cin : in std_logic;
        cout, s: out std_logic);
end component;
```

```
signal carry_bit: std_logic_vector(4 downto 0);
```

```
begin
```

```
    four_adder : for i in 0 to 3 generate
        add_one_bit: full_adder
            port map (a=>a(i), b=>b(i), cin=>carry_bit(i),
                    cout=>carry_bit(i+1), s=>s(i));
    end generate four_adder;
```

} FOR statement

```
    carry_bit(0) <= cin;
    cout <= carry_bit(4);
```

```
end arch1;
```

# Operators in VHDL

(Not an exhaustive list)

- Logical (for Boolean or bit operations)
  - ◆ and, or, nand, nor, xor, not
- Relational
  - ◆ =, /=, <, <=, >, >=
- Arithmetic
  - ◆ +, -, abs, mod, rem, \*, /
- Concatenate
  - ◆ & (example `c <= a & b;`)

# Concatenation operator (&)

- Used for linking together bits and vectors to build a longer vector
- Examples:

```
signal a: std_logic_vector(3 downto 0) := "1001";  
signal b: std_logic_vector(6 downto 0);
```

```
b <= "101" & a;           -- Result: b = "1011001"
```

```
a <= '1' & a(3 downto 1); -- Result: a = "1100"
```

```
b <= '1' & "11" & "0000"; -- Result: b = "1110000";
```

# Two assignment operators:

- Variable assignment (:=)
  - ◆ Syntax: variable := value;
  - ◆ Immediately assigns new value to a variable within a process
  - ◆ Also to initialize signals, variables, constants
- Signal assignment (<=)
  - ◆ Syntax: signal <= value [after time];
  - ◆ Delayed assignment of new value to a signal
  - ◆ If used in a process, signal value changes at the end of the process.

# Assignment operators used in a process (example)

```
parity_calc : process (a,b)

    variable temp: std_logic;

begin

    temp := '1';           -- sequential code!
    temp := temp xor a;
    temp := temp xor b;

    parity_out <= temp;    -- Assign the result to a signal

end process;
```




# Sequential logic

# Sequential logic

- Sequential code must be written inside processes
- Registers (flip-flops) created by making a process dependent on a “clock” signal
- Multiple ways to code conditional statements
  - ◆ “if...then” is very common
    - ✦ Good for clock statements and asynchronous behavior
  - ◆ “case” is useful for coding state machines
  - ◆ “wait until...” also possible
    - ✦ But not recommended for synthesis
 
# Latches vs flip-flops

- Both rely on a clock signal
- Latches change outputs on a clock level (high or low)
- Flip-flop outputs change on a clock edge (rising or falling)





 
# Example: D-latch


(not recommended for use in FPGAs)

```
process (CLK)
  begin
    if CLK='1' then
      Q <= D;
    else
      -- Don't do anything
    end if;
  end process;
```


 
# Or more concisely...

```
process (CLK)
begin
  if CLK='1' then
    Q <= D;
  end if;
end process;
```




The empty 'else' condition is implied
 
# D flip-flop

Using native syntax:

```
process (CLK)
begin
  if CLK'event and CLK='1' then
    Q <= D;
  end if;
end process;
```



Rising edge




# D flip-flop

Using IEEE 1164 std\_logic syntax:  
(recommended)

```
process (CLK)
  begin
    if rising_edge(CLK) then
      Q <= D;
    end if;
  end process;
```

(can also use falling\_edge)

 


# Common sequential designs

- Finite State Machine (FSM)
  - ◆ State information saved from previous operations, used in next operation
- Pipelined algorithms
  - ◆ Sequential operations performed on data in multiple steps

# Pipelined algorithms


Input registers

Output register

 


Single-stage summation

# Pipelined algorithms

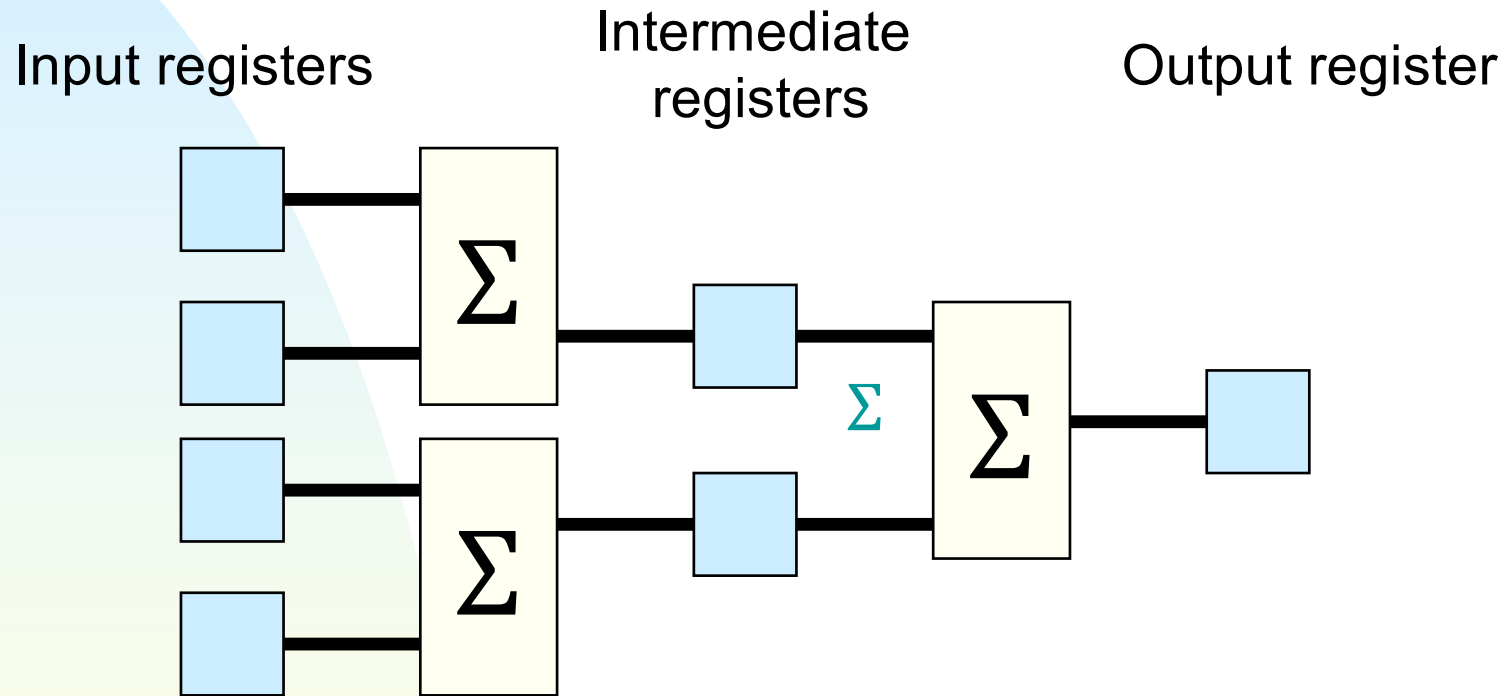

Multi-stage summation:  
Faster clock speed  
(but longer latency)


# FSM types

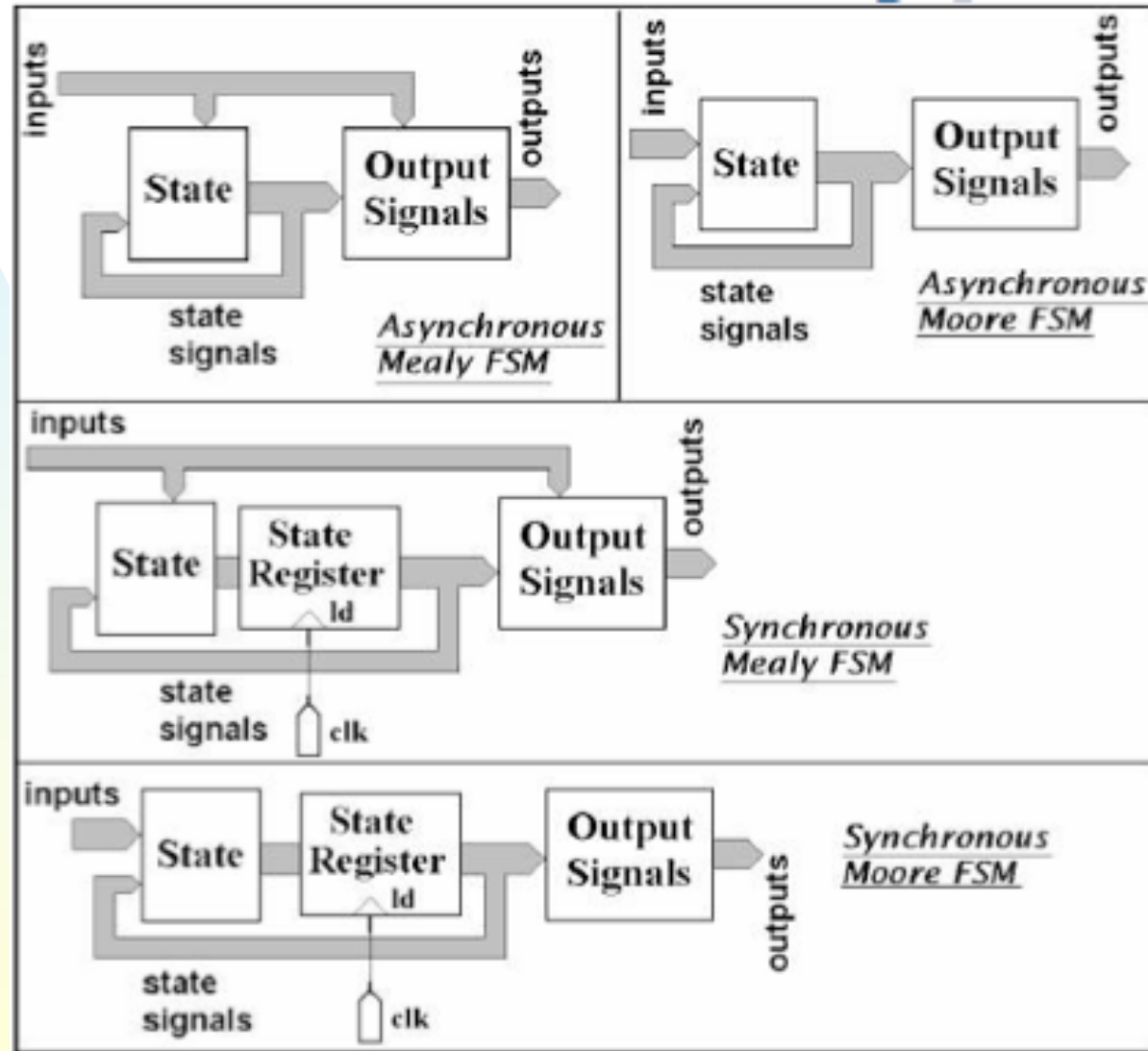



 
# Review: synchronous Moore FSM

- Let Z equal 1 after inputs X and Y are equal 3 times in a row:



x =	0	1	1	0	0	1	1	1	0	1	0	0	0	1	0	1	0	1	1	0	1	0	0	0	0	0	1	
y =	1	1	1	0	1	1	1	1	0	1	1	0	0	1	0	1	0	1	1	0	1	0	1	0	1	1	1	1
z =	0	0	0	1	0	0	0	1	0	0	0	0	0	0	1	0	0	1	0	0	1	0	0	0	0	0	0	0

# Flow chart for the FSM

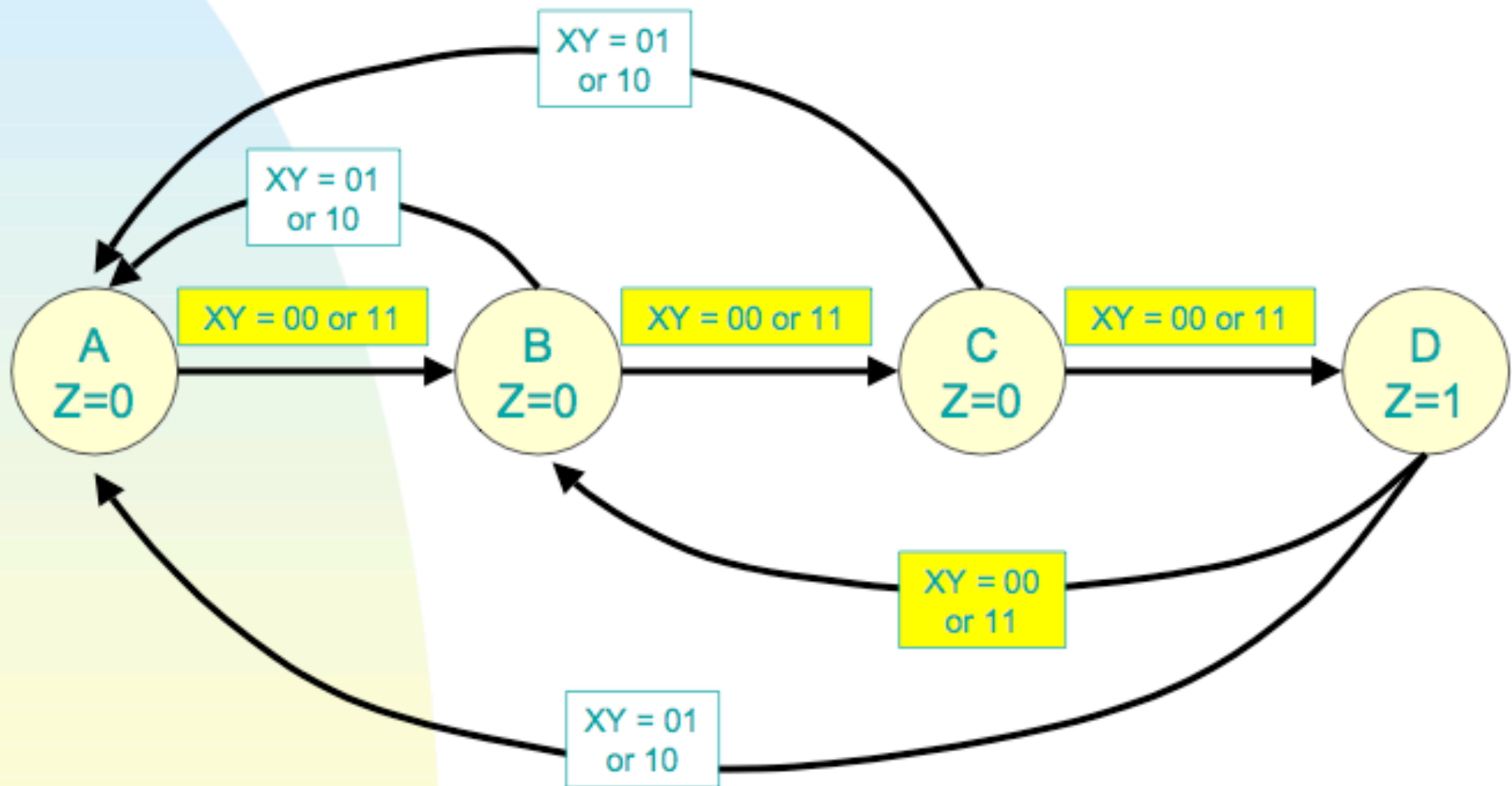

# Entity for the FSM:

```
entity FSM is
port (x:  in std_logic;
      y:  in std_logic;
      clk: in std_logic;
      z:  out std_logic
      );
end FSM;
```

# Behavioral architecture

architecture behav of FSM is

```
signal state: std_logic_vector (1 downto 0);
```

```
begin
```

```
reg1 : process (clk, x, y, state)
```

```
begin
```

```
  if rising_edge(clk) then
```

```
    case state is
```

```
      when "00" =>
```

```
        if (x = y) then state <= "01"; else state <= "00";
```

```
        end if;
```

```
      when "01" =>
```

```
        if (x = y) then state <= "10"; else state <= "00";
```

```
        end if;
```

```
      when "10" =>
```

```
        if (x = y) then state <= "11"; else state <= "00";
```

```
        end if;
```

```
      when others =>
```

```
        if (x = y) then state <= "01"; else state <= "00";
```

```
        end if;
```

```
    end case;
```

```
  end if;
```

```
end process;
```

```
z <= state(1) and state(0);
```

```
end behav;
```

If..then with a clock edge implements the flip-flops

Clear description using "case"

} Output

# Assignment operator: <=

- Implies a time delay from right-hand side to the left-hand side of the operator
  - ◆ Signal value is updated at “end process”
- If signal assignment depends on a clock edge, a flip-flop is implemented.
  - ◆  $\text{state (after clock edge)} \leq \text{state (before clock edge)}$

# Order is not important for concurrent statements

architecture behav of FSM is

```
signal state: std_logic_vector (1 downto 0);
```

```
begin
```

```
z <= state(1) and state(0);
```

} Output is concurrent with the process

```
reg1 : process (clk, x, y, state)
```

```
begin
```

```
if rising_edge(clk) then
```

```
case state is
```

```
when "00" =>
```

```
if (x = y) then state <= "01"; else state <= "00";
```

```
end if;
```

```
when "01" =>
```

```
if (x = y) then state <= "10"; else state <= "00";
```

```
end if;
```

```
when "10" =>
```

```
if (x = y) then state <= "11"; else state <= "00";
```

```
end if;
```

```
when others =>
```

```
if (x = y) then state <= "01"; else state <= "00";
```

```
end if;
```

```
end case;
```

```
end if;
```

```
end process;
```

```
end behav;
```

# Order not important in concurrent code

```
architecture rtl of FSM is
```

```
signal state : std_logic_vector (1 downto 0);
```

```
begin
```

```
z <= state(1) and state(0);
```

} Concurrent with the process

```
reg1: process (clk, x, y, state)
```

```
begin
```

```
if (rising_edge(clk)) then
```

```
state(1) <= (not (x xor y)) and (state(1) xor state(0));
```

```
state(0) <= (not (x xor y)) and (state(1) or not (state(0)));
```

```
end if;
```

```
end process;
```

```
end rtl;
```

# Example: 4-bit counter (entity)

```
library ieee ;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all; -- New library!

entity counter is

    generic(n: natural := 4); -- Width of the counter
    port(clock:      in std_logic;
          clear:     in std_logic;
          Q:         out std_logic_vector(n-1 downto 0)
    );
end counter;
```



# 4-bit counter (architecture)

architecture behv of counter is

```
    signal Count: std_logic_vector(n-1 downto 0);

begin

    process(clock, clear)
    begin
        if clear = '1' then
            Count <= Count - Count;
        elsif rising_edge(clock) then
            Count <= Count + 1;
        end if;
    end process;

    Q <= Count; } Output

end behv;
```

Asynchronous reset

Synchronous with clock

Unsigned + and - operations

# Another way to write it:

architecture behv of counter is

```
signal Count: std_logic_vector(n-1 downto 0);
```

```
begin
```

```
process(clock, clear)
```

```
begin
```

```
if clear = '1' then
```

```
Count <= (others => '0');
```

```
elsif rising_edge(clock) then
```

```
Count <= Count + 1;
```


```
end if;
```

```
end process;
```

```
Q <= Count; } Output
```

```
end behv;
```

Fill all elements  
of vector with '0'



Unsigned + and - operations



# Why use Count internally, instead of just using Q?

- Q is an output of the entity
- An architecture can only write to an output
  - ◆ Not read from it!
- So here we use an internal signal (Count)
  - ◆ Count can be both written and read.
  - ◆ Output Q is then set to the value of Count
  - ◆ Signals like count are sometimes called buffers

# Process sensitivities

- Sensitivity list is part of a process declaration
- Process outputs can change when at least one signal in the sensitivity list changes
- Safest to include all input signals in the list
  - ◆ Not necessary, but synthesis may give fewer warnings...
- Missing (important) sensitivities are discovered most often in simulation

# Sensitivity example: FSM

```
reg1: process (clk)
begin
    if (rising_edge(clk)) then state <= next_state;
    end if;
end process;
```

This works because “clk” is always changing in every cycle.  
But “next\_state” can also change the output!

# Example: FSM

```
reg1: process (clk, next_state)
begin
    if (rising_edge(clk)) then state <= next_state;
    end if;
end process;
```

This is a “safer” way to do the same thing  
(or at least get fewer warnings)

# Example: counter


```
process(clock, clear)
begin
  if clear = '1' then
    Count <= (others => '0');
  elsif (clock='1' and clock'event) then
    Count <= Count + 1;
  end if;
end process;
```

`clear` is a required sensitivity, because it does not have to change at the same time as `clock`.
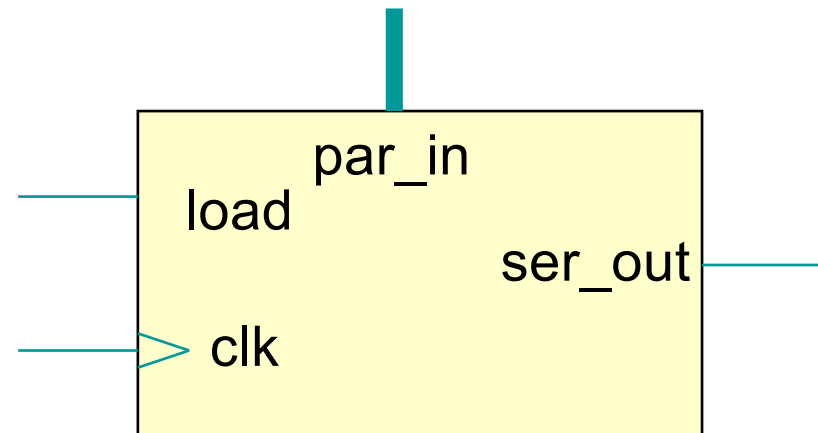
# Example: simple shift register

Function: load a parallel value, then circular shift to the right, with the least significant bit sent to ser\_out

```
entity simple_sr is
  port(par_in:   in std_logic_vector(3 downto 0);
        load:    in std_logic;
        clk:     in std_logic;
        ser_out: out std_logic
  );
end simple_sr;
```






# simple\_sr architecture

architecture behav of simple\_sr is

```
signal val : std_logic_vector(3 downto 0);
begin
reg1: process (clk, load, par_in, val)
  begin
    if (rising_edge(clk)) then
      case load is
        when '1' => val <= par_in; -- load parallel value
        when others => val <= val(0) & val(3 downto 1); -- shift
      end case;
    end if;
  end process;

  ser_out <= val(0); -- Output
end behav;
```

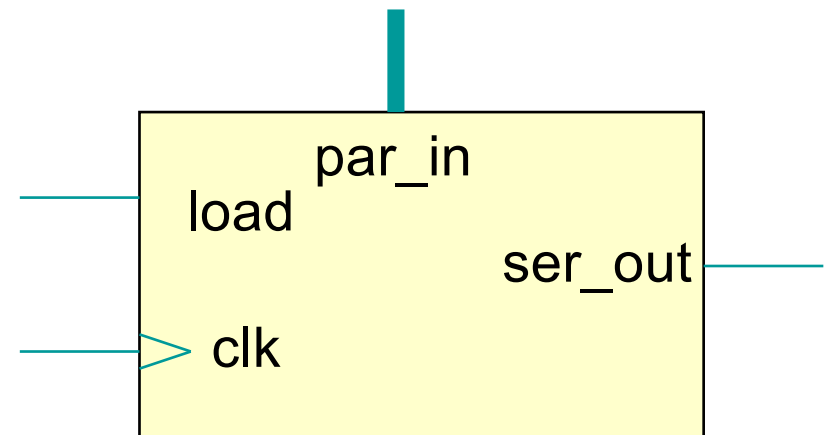Use "&" operator to move the LSB up to MSB, and shift down the top three bits



# Be careful to avoid extra registers

architecture behav3 of simple\_sr is

```
signal val : std_logic_vector(3 downto 0);
```

```
begin
```

```
  reg1: process (clk)
```

```
  begin
```

```
    if (rising_edge(clk)) then
```

```
      case load is
```

```
        when '1' => val <= par_in;
```

```
        when others => val <= val(0)
          & val(3 downto 1);
```

```
      end case;
```

```
      ser_out <= val(0);
```

```
    end if;
```

```
  end process;
```

```
end behav2;
```

} Registered

← Extra register added to Output!

# What happens when you do this?

- Signals `val` and `ser_out` are updated on the same rising edge of the clock (after the process is ended)
- So `ser_out` is updated with the contents of `val` from the previous clock cycle.
- Algorithm has an extra clock cycle of latency!



Keep track of timing!

# Serial vs parallel arithmetic


- Example: n-bit Adder

- ◆ Parallel


- ◆ A and B are vectors with width  $n$
- ◆ Sum is vector with width  $n$  (plus carry)
- ◆ Summation done in one clock cycle

- ◆ Serial

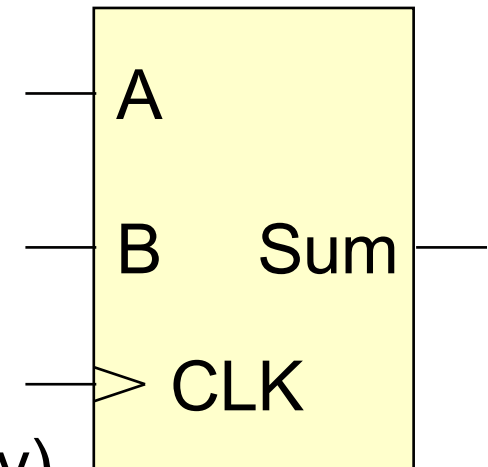- ◆ A and B are single-bit inputs
- ◆ Input data arrives in  $n$  cycles, LSB first
- ◆ Output data leaves in  $n$  cycles, LSB first



# Serial Adder

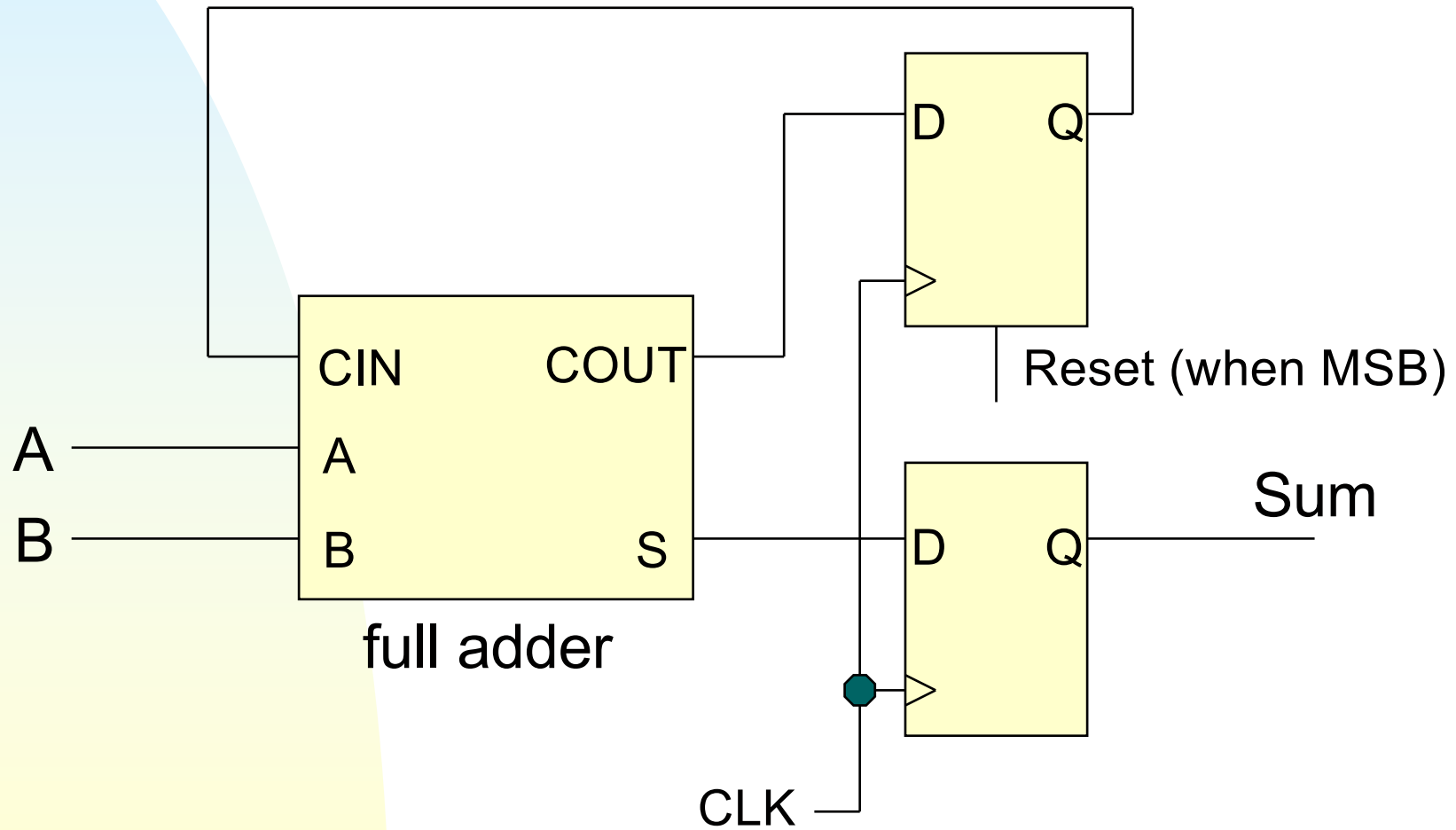

# Why use serial arithmetic?

- Size
  - ◆ Parallel adder needs  $n$  full adders
  - ◆ Serial adder needs only 1 full adder
- Speed
  - ◆ Shorter carry chains mean less propagation delay
  - ◆ This allows serial adders to run at higher clock speeds  
(but longer latency)
- Serial adders can be useful for
  - ◆ Pipelined algorithms with many steps
  - ◆ Designs with serial input/output data

# Lab 2 (next Monday)

- Produce a bit-serial adder
  - ◆ Design components
  - ◆ Test components individually
  - ◆ Assemble into full design
- Synthesize and implement
- Test on the developer board

# Before the lab

- Read through Lab 2 writeup
- Think about components you will need, and how to implement them
- Try to write some sample code