



FYSIKUM

Digital System Construction - 1

Lecture 5: Designing for FPGA

Frequently-asked questions/
Good design practice

Timing

Types and records in VHDL

Lab 4 intro: digital stopwatch

Frequently asked questions

- Do functions/processes “remember” the values of variables?
 - ◆ Yes!
 - ✦ For example, a "counter" variable remembers the last count.
 - ◆ Different from software, where function variables can be re-initialized each time the function is called
- Signal/port names:
 - ◆ Can a signal in an architecture can have the same name as a port of one of the components?
 - ◆ Yes!
 - ✦ `port map (select => select,);`
 - ◆ Good practice to propagate common signals throughout the design:
 - ✦ `reset, clock, ...`

Frequently asked questions

- How do you use (read from) the value of an output port within the architecture?
 - ◆ You can't read outputs directly.
 - ◆ If you need to, create a signal for internal use, and then assign that signal to the output port:
 - ✦

```
int_buf <= (int_buf and enable);
```

```
output <= int_buf;
```
 - ◆ Another method is to declare a port as bi-directional (`inout` instead of `out`)
 - ✦ Not recommended unless a bi-directional port is really needed for your design

Signals versus variables

- Example: counting with a signal:

```
architecture behav of clk_div is
    signal count: std_logic_vector (3 downto 0);
    signal slowck : std_logic := '0';

begin
    cproc : process(clk)
    begin
        if rising_edge(clk) then
            if (count = "1111") then
                count <= "0000";
                slowck <= not slowck;
            else
                count <= count + 1;
            end if;
        end if;
    end process;
end behav;
```

count is only updated
once in the process

Signals versus variables

- Counting with a variable:

```
architecture behav of clk_div is
    signal slowck : std_logic := '0';


begin
    cproc : process(clk)
        variable count : integer := 0;
    begin
        if rising_edge(clk) then
            count := count + 1;
            if (count > 15) then
                count := 0;
                slowck <= not slowck;
            end if;
        end if;
    end process;
end behav;
```

Only one signal
needed outside
the process


count can be changed
more than once with
variable assignment (**:=**)

Component port maps

- Good to connect named signals to ports
 - ◆ Even if they are not used elsewhere, you can follow them while simulating
 - ◆ Helps avoid accidental connections
- Inputs must always be connected
- Outputs don't need to be connected
 - ◆ But unused logic is trimmed anyway
 - ◆ Can also use: `Par_out => open`
- Connect outputs to unique signals
 - ◆ Avoid multiple drivers
 - ◆ Exception: Tri-state ('Z') connection to a bus

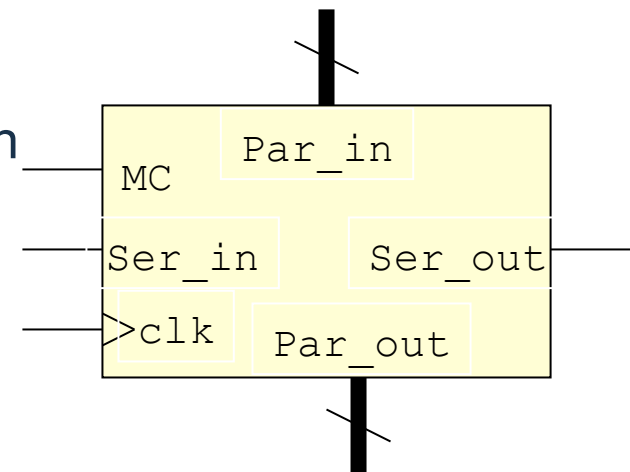

Bi-directional signals (with tri-state)

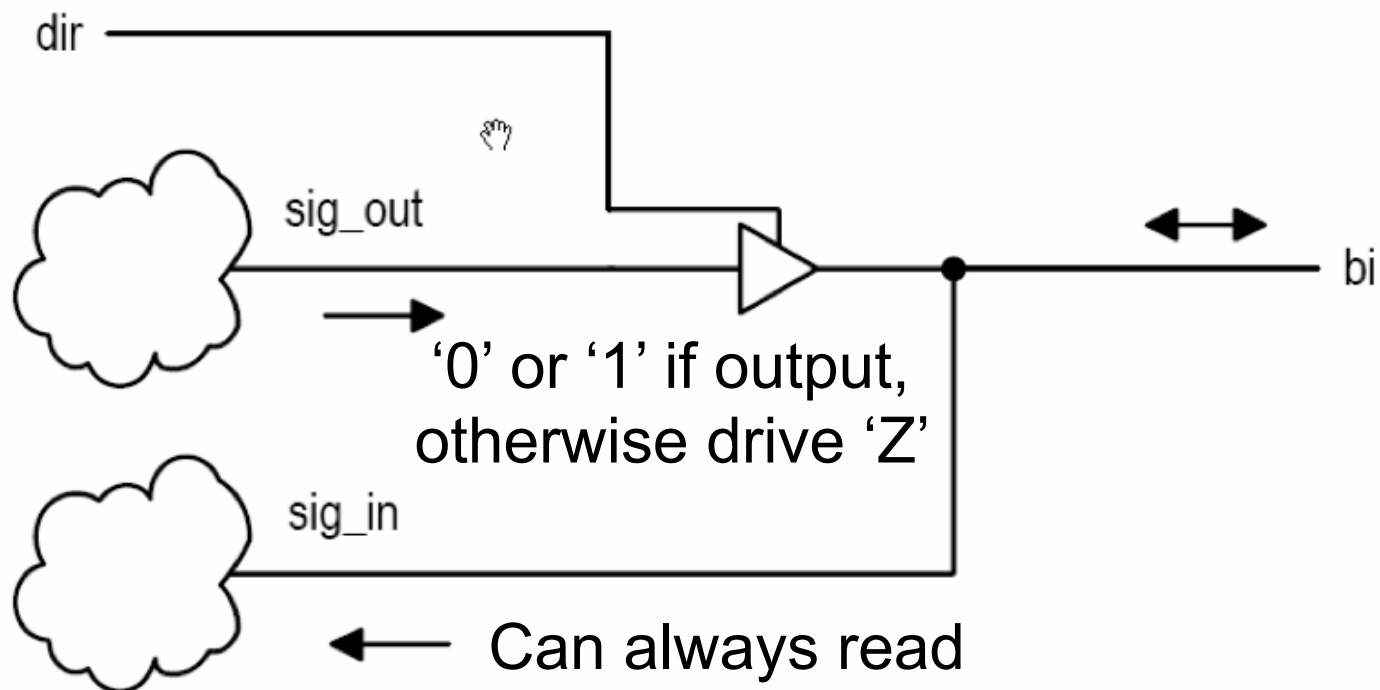


Implementing in VHDL

```
entity bus_IO is
    Port(Din:  in      std_logic;
          Dout: out      std_logic;
          IO_pin: inout std_logic;
          wr_en: in      std_logic );
end bus_IO


.....

buffer_rw : process (Din, IOpin, wr_en) -- can also be clocked
begin
    if (wr_en) then
        IO_pin <= 'Z'; -- high impedance if not driving
    else
        IO_pin <= Dout;
    end if;
    Din <= IO_pin;      -- Always can read
end process;
```


Tri-state bus example

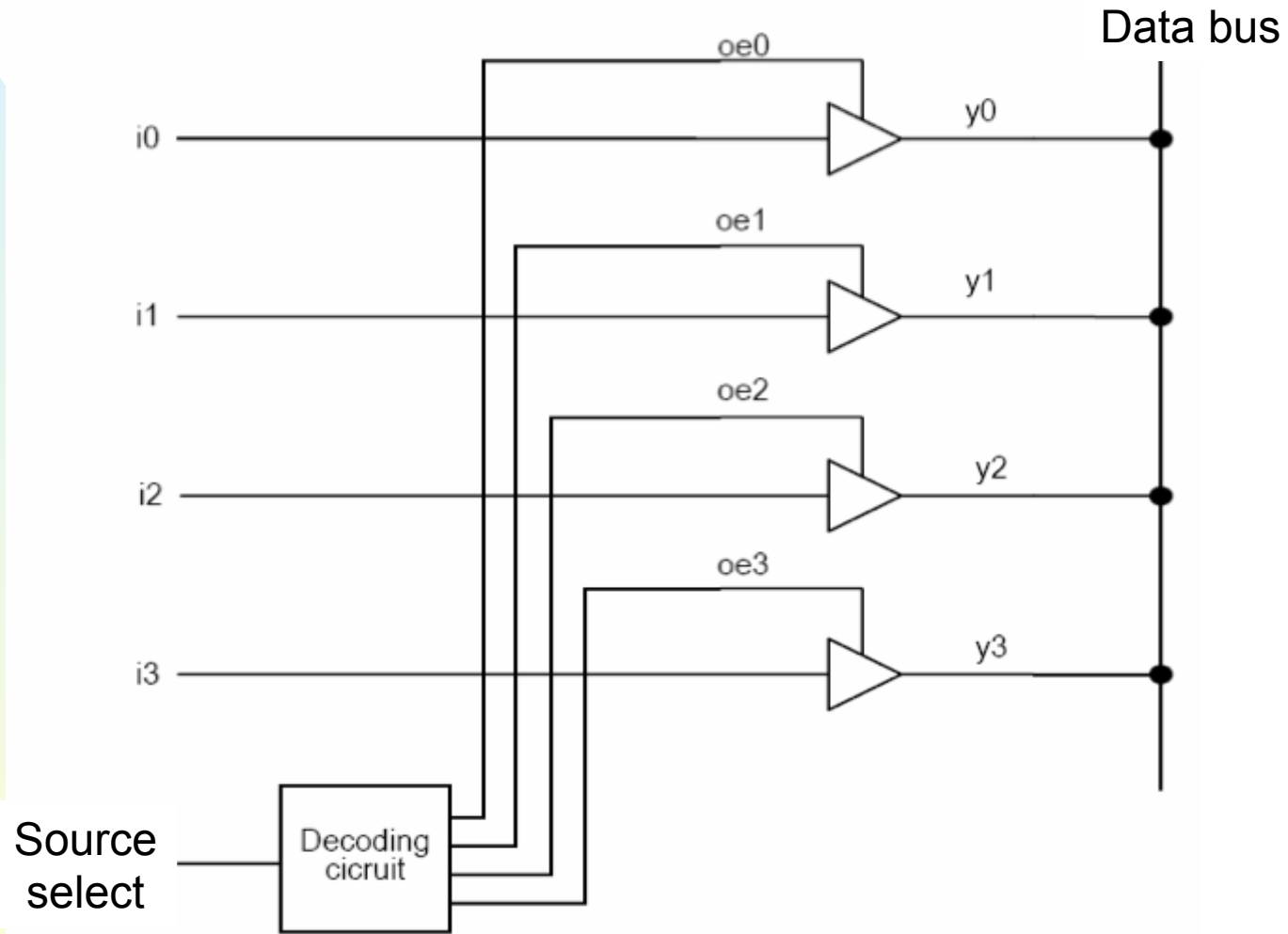


Be careful with timing...

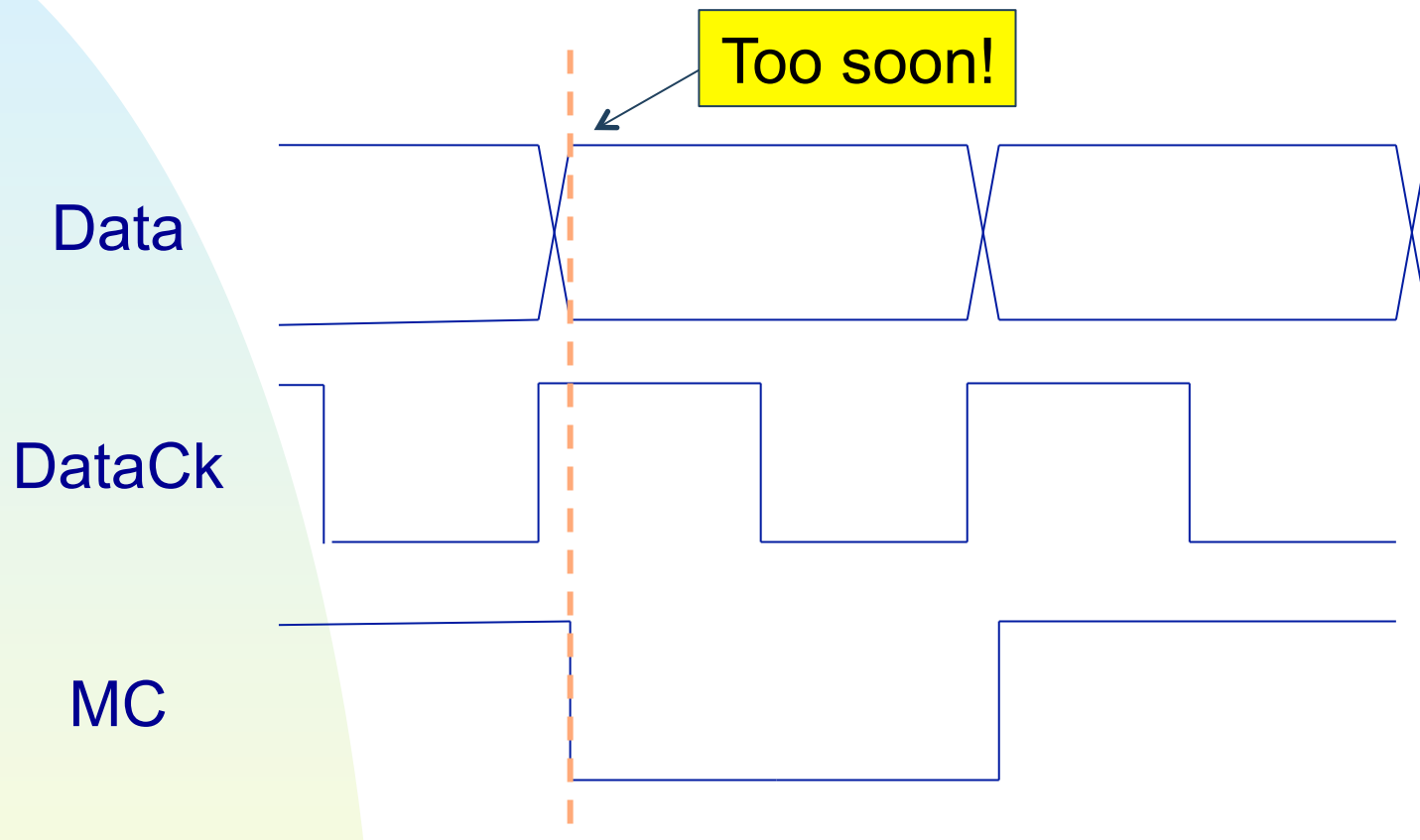

```
if falling_edge(MC) then newdata <= data;
```

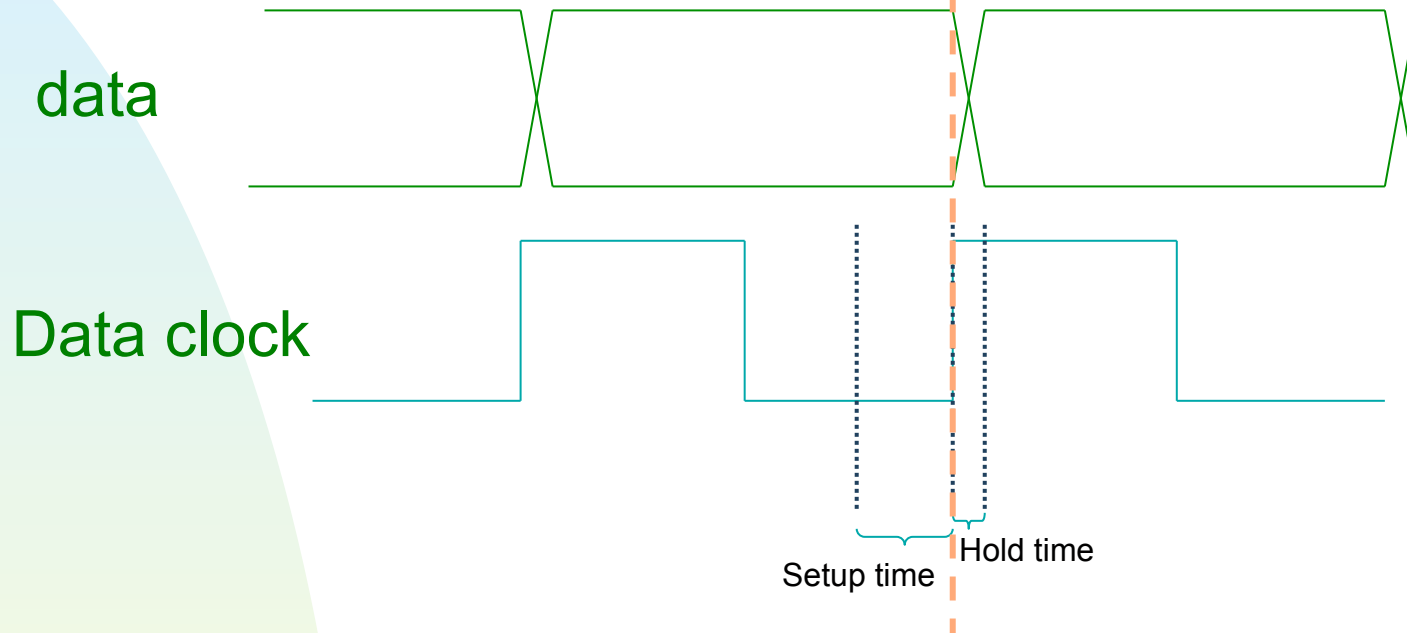
Flip-flops have minimum setup/hold times:



Setup time: Data must be stable before clock edge

Hold time: Time for flip-flop output to stabilize (short)


A better approach:

 

```
if rising_edge(clock) and MC='0' then  
    newdata <= data;
```


Even this can be risky:

 New data can take some time to become valid (propagation delays, setup/hold times, etc)



```
if falling_edge(DataCk) then newdata <= data;
```

"Gated Clocks"

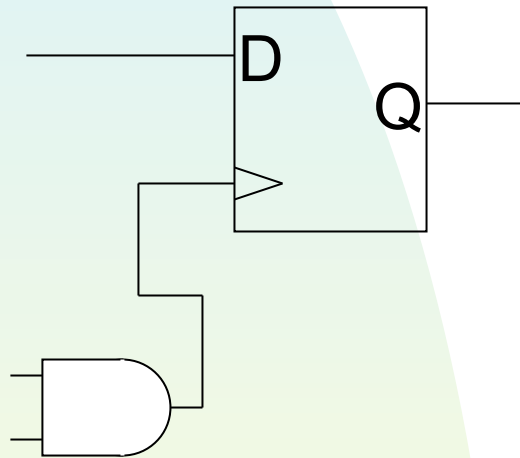

- Flip-flops driven by combinatorial logic
- Disadvantages:
 - ◆ Timing differences between FFs driven by the same source (propagation)
 - ◆ Unpredictable: hard to get good synthesis performance
 - ◆ Gated clock edge degraded as more FFs load the same driver
- If you need to use a logic-derived signal to drive flip-flops, you can:
 - ◆ Pass the logic output through a flip-flop (driven by another clock in your design), or
 - ◆ Distribute the new timing signal through a global (or regional) FPGA clock buffer

Global clock buffers

- Distribute selected timing signals synchronously
- Inputs can be external timing signals, internally synthesized clocks, gated signals, etc
- Can use Clocking Wizard in IP Catalog
- 7-series global buffer in pure VHDL:

```
Library UNISIM
use UNISIM.vcomponents.all

component bufg -- (or ibufg)
  port (
    I: in std_logic;
    O: out std_logic);
end component;
```


Good clocking practice

- Drive flip-flops with global clocks
 - ◆ Use gated logic to “enable” clock
- Bring high-quality clocks to the FPGA
 - ◆ Crystal oscillators have low jitter
 - ◆ “Jitter cleaner” circuits can improve performance of non-crystal clocks
- Use designated clock pins, if available
 - ◆ Designed for optimal input to global buffers
- Distribute internally-generated clocks via global or regional clock buffers as well


Don't blindly trust the synthesis!

- Modern tools very powerful, but not perfect
 - ◆ Some HDL descriptions can lead to non-optimal results
 - ✦ Synthesis software doesn't know exactly what you want
 - ✦ Optimal solution can't be derived, optimization process is an iterative search in a large "space" of possible solutions
 - ✦ Good HDL code gives a good starting point for that search
- Pay attention to errors and warnings
 - ◆ Even buggy designs can synthesize, but not work right!
 - ◆ Check timing/mapping reports
 - ✦ Constraints met? Reasonable resource use?
- Check RTL schematics in ISE
 - ◆ Structure look like you expect?

 Example: XOR cascading chain vs. tree structure




Cascading chain

 


Tree structure

 Can choose to optimize for speed / area / both



Less logic
(area)

 

Smaller delay
(speed)



Types in VHDL

Constants and variables

```
constant number_of_bytes : integer := 4;  
constant number_of_bits : integer := 8*number_of_bytes;  
constant e : real := 2.718281828;  
constant prop_delay : time := 3 ns;  
  
variable index: integer := 0;  
variable start, finish : time := 0 ns;
```

- Constants can be declared globally (in architecture) or within sequential code (process, procedure, functions)
 - Generally declared with a value
- Variables are declared in a piece of sequential code; not normally visible outside that process, etc.

Scalar types

- A scalar type has discrete values
 - ◆ No composite elements
- All values are ordered
 - ◆ Each value has an implicit position number
 - ◆ Predefined relational operators work
- Scalar types include:
 - ◆ Numeric (integer, floating point)
 - ◆ Physical (for example, time)
 - ◆ Enumerated types
- `integer` is a scalar type representing all whole numbers representable on the host computer

Scalar types

Example of declaration and use in a package

```
type apples is range 0 to 100;  
  
package int_types is  
    type small_int is range 0 to 255;  
end package int_types;  
  
use work.int_types.all;  
entity smaller_adder is  
    port (a, b : in small_int;  
          s : out small_int);  
end entity small_adder;
```

Floating-point types

Not usually used for synthesis

```
type input_level is range -10.0 to 10.0;  
type probability is range 0.0 to 1.0;
```

```
variable input_A: input_level;
```


Assignments use variables or constants of same type

```
type day_of_month is range 0 to 31;  
type year is range 0 to 2100;
```

```
variable today: day_of_month := 19;  
variable start_year: year := 2005;
```

Not legal to make this assignment:

```
start_year := today;
```

Integer/vector conversion in std_logic_unsigned

```
use ieee.std_logic_unsigned.all;  
use ieee.std_logic_arith.conv_std_logic_vector;  
  
signal vector : std_logic_vector (v_width downto 0);  
integer int_var;  
  
--std_logic to integer:  
  
int_var <= conv_integer(vector);  
  
--integer to std_logic:  
  
vector <= conv_std_logic_vector(int_var, vector'length);
```

data types have
attributes



Some useful VHDL attributes

- `type'pos(value)` -- integer position of value in the type
- `type'val(i)` -- value of type at integer position I

- `array'length` – number of elements in an array/vector
- `array'range` -- range of an array/vector
- `array'low` -- lowest subscript of an array/vector
- `Array'high` -- highest subscript of an array/vector

- `signal'event` -- true if signal changes value

(Not an exhaustive list...)

Enumerated types

```
type alu_function is (disable, pass, add, subtract,  
                        multiply, divide);  
type octal_digit is ('0','1','2','3','4','5','6','7');  
  
variable alu_op: alu_function;  
variable last_digit: octal_digit := '1';  
  
alu_op      :=      subtract;  
last_digit  :=      '7';
```

Enumerated type attributes

```
type alu_function is (disable, pass, add, subtract,  
                    multiply, divide);
```

- Each enumeration literal has an integer "position number" (0, 1, 2, 3, etc.)
- The first (left-most) enumeration literal has position 0, the next has position 1, etc.

◆ `int_variable <= alu_function'pos(pass);`

◆ `alu_option <= alu_function'val(3);`

subtract

Data types: Record

- Useful for bundling groups of signals
 - ◆ Especially different signal types
- Example: CPU memory bus:
 - ◆ `address()`, `data()` -- vectors
 - ◆ `read_en`, `write_en`, `chip_sel` -- bits
 - ◆ `clock`, `reset` – timing

Declaring and using records

```
type memory_bus is record
    address, data      : std_logic_vector(15 downto 0);
    rd_en, wr_en, c_sel : std_logic;
    clk, reset         : std_logic;
end record;
```


```
signal address1      : std_logic_vector(15 downto 0);
signal bus1, bus2    : memory_bus;
```

```
bus1.address <= address1; -- Assign signal to record element
```

```
bus1.wr_en <= '1'; -- Assign value to record element
```

```
bus2.data <= bus1.data; -- Copy part of a record
```

```
bus2 <= bus1; -- Copy entire record
```



**Record example (ATLAS):
L1Calo trigger topology
processor (L1Topo)**

Package: L1TopoDataTypes.vhd

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
Package L1TopoDataTypes is
```

```
  type ClusterTOB is record
```

```
    Et : std_logic_vector (7 downto 0);  
    isol: std_logic_vector (4 downto 0);  
    eta: std_logic_vector (5 downto 0);  
    phi: std_logic_vector (5 downto 0);
```

```
  end record;
```

```
  type JetTOB is record
```

```
    Et1 : std_logic_vector (8 downto 0);  
    Et2: std_logic_vector (9 downto 0);  
    eta: std_logic_vector (4 downto 0);  
    phi: std_logic_vector (4 downto 0);
```

```
  end record;
```

```
  type ClusterArray is array (natural range <>) of ClusterTOB;
```

```
  type JetArray is array (natural range <>) of JetTOB;
```

```
-- After selection and sorting, use generic type for all TOBs.
```

```
  type GenericTOB is record
```

```
    Et : std_logic_vector (9 downto 0); -- Pad unused bits with zeros  
    eta: std_logic_vector (5 downto 0);  
    phi: std_logic_vector (5 downto 0);
```

```
  end record;
```

```
  type TOBArray is array (natural range <>) of GenericTOB;
```

```
end;
```

Can declare with
any width

Using in an algorithm:

```
library ieee;
use ieee.std_logic_1164.all;
use work.L1TopoDataTypes.all;

entity DeltaPhiIncl1 is
    generic(InputWidth      : integer := 8);
    port(
        Tob          : in  TOBArray(InputWidth - 1 downto 0);
        Parameters  : in  ParameterArray;
        ClockBus    : in  std_logic_vector(2 downto 0);
        Results     : out std_logic_vector(NResultBits - 1 downto 0));
end DeltaPhiIncl1;

. . . . .

    deltaPhi_calc1 : for i in 0 to (maxCount - 2) generate
        deltaPhi_calc2 : for j in (i + 1) to (maxCount - 1) generate
            dphiCalc_inst : entity work.DeltaPhiCalc
                port map(
                    phi1In      => Tob(i).phi,
                    phi2In      => Tob(j).phi,
                    deltaPhiOut => deltaPhi(i)(j)
                );
        end generate;
    end generate;
```

Compare all
TOB pairs




Lab 4: Digital counter (stopwatch)


Basic stopwatch function

- Input: single pushbutton
- Output: 7-segment display
 - ◆ (time to 1/100 second)
- Behavior:
 - ◆ Push once: start timer
 - ◆ Push again: stop, display time
 - ◆ Push again: clear timer

State diagram (simplified)

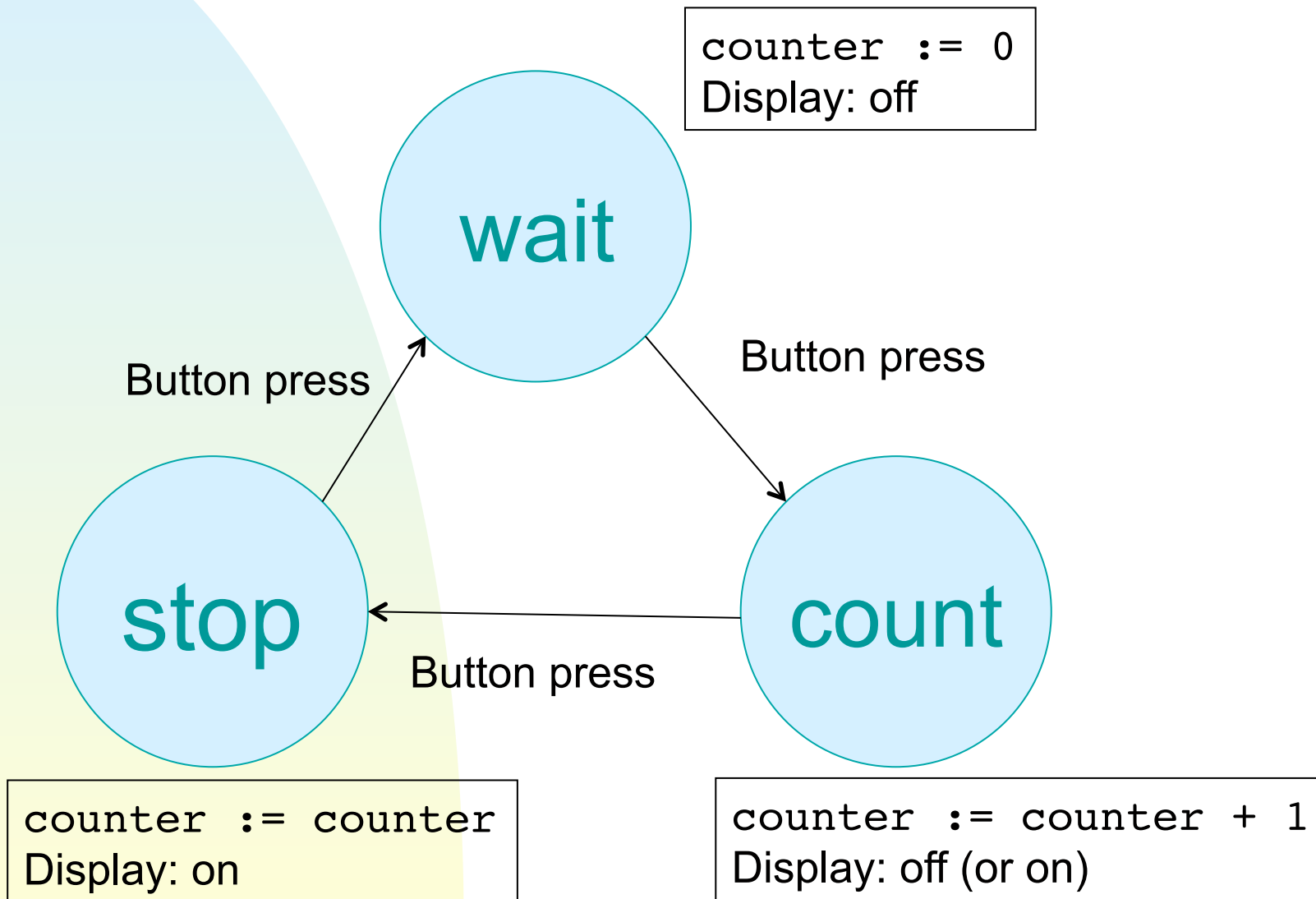

Clock divider

 


- Problem:
 - ◆ FPGA has a fast clock (e.g. 100 MHz)
 - ◆ We need a slow clock (100 Hz)
- Solution: a clock divider
 - ◆ Internally a counter, clocked at 100 MHz
 - ◆ Reset counter to zero every 0.01 s
 - ✦ Max count $(100.000.000 / 100) = 1.000.000$
- Good to have a symmetric output:
 - ◆ If count $< (1.000.000 / 2)$ then output $\leq '1'$
 - ◆ Otherwise output $\leq '0'$;

'Debouncing' a button


(not needed for lab)

One approach:
use a counter

Electrical signal from button:

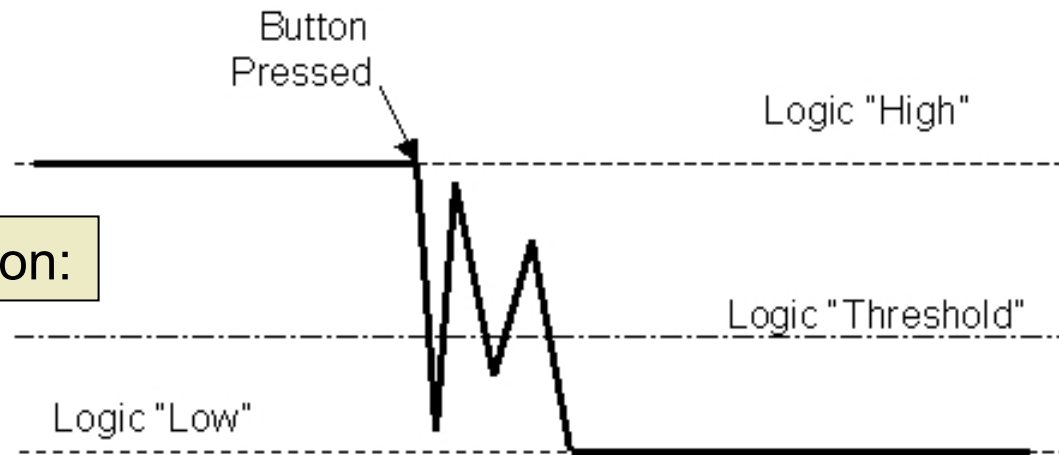


Logical signal seen at FPGA input:

 

Buttons on your lab boards are passively debounced (capacitor)

 Debounce circuit waits a few clock cycles before the output is allowed to fall:




Stopwatch block diagram


Button




100 MHz

 

100 Hz

 

7-segment
hex display

 

100 MHz